

Community Institute of Management studies

Computer Organization and Architecture

Answer the following

1.Convert the following:

i) $7562_{(10)} = \text{-----}_{(16)}$

vi) $673.124_{(8)} = \text{-----}_{(2)}$

ii) $1110101_{(2)} = \text{-----}_{(10)}$

vii) $123.6875_{(10)} = \text{-----}_{(16)}$

iii) $F3A7_{(16)} = \text{-----}_{(8)}$

viii) $1010.011_{(2)} = \text{-----}_{(10)}$

iv) $FADE_{(16)} = \text{-----}_{(10)}$

ix) $BDA.D4_{(16)} = \text{-----}_{(8)}$

v) $3527_{(8)} = \text{-----}_{(16)}$

x) $0.6875_{(10)} = \text{-----}_{(2)}$

2.i) Subtract $73_{(10)}$ from $28_{(10)}$ using 2's complement method

ii) using 2's complement subtract 1010100 from 1000011

3.With a neat circuit diagram and truth table, explain the working of Full Adder

4.Construct a 4 to 1 line multiplexer using logic gates. Explain its working procedure

5.Implement the following Boolean function using 8:1 Multiplexer

$$F(A B C D) \sum m(1,3,5,6,9,11,13,15)$$

6.Simplify $F(A B C D) = \sum m(1,2,6,11,15) + \sum d(0,3,9,10,14)$ using K map and write the circuit diagram for the simplified expression

7.Explain error detection and correction using Hamming code

8.Explain 2 bit binary counter

9.Explain Register reference instructions

10.Explain Memory reference instructions